

Hints:

① Look @ .out and .cmp files!


② You can send the same output multiple places!

eg



Mux16(....., out=out, out=Q, out[15]=...)

Memory.


S-R latch.

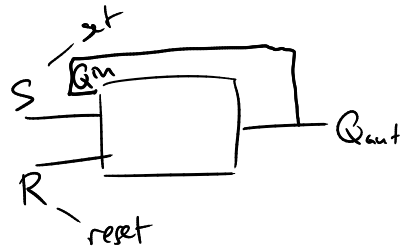


S	R	Qout
0	0	(stay same)
1	0	1
0	1	0

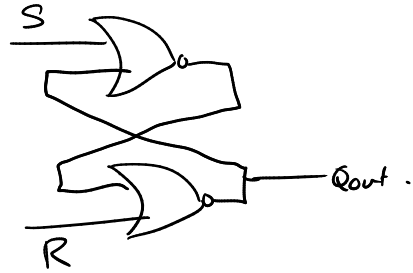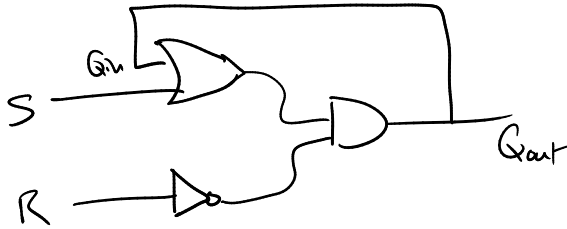

D latch (data latch)

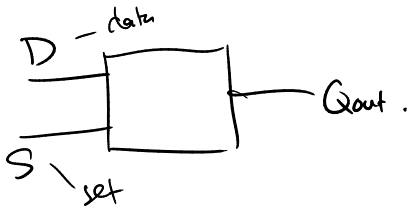


D	S	Qout
?	0	stay same
?	1	D

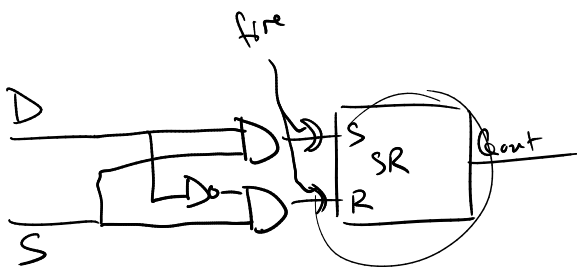


Problem: timing/synchronization!


Solution: clock.

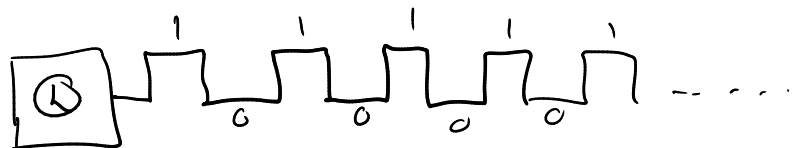


Clocked D-latch:

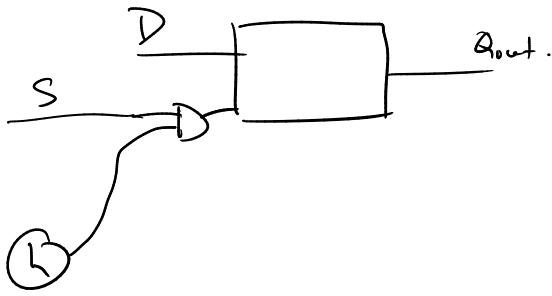

Better - updates when clock goes 0 → 1.

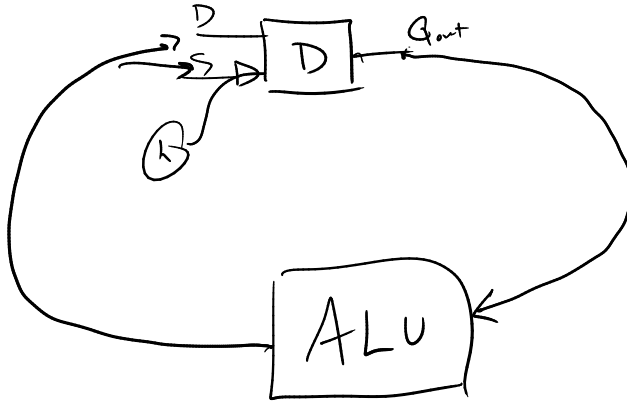

D flip-flop

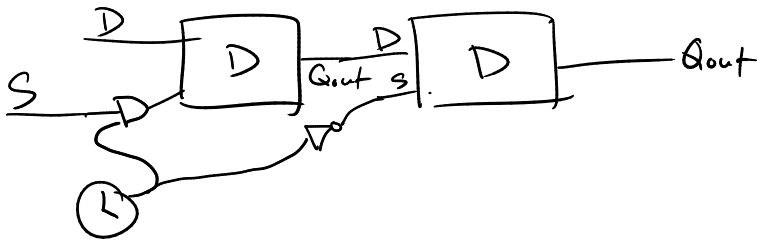

RAM = Random Access Memory

↳ can access any port equally fast.

Every location has an address which is an integer.

Hack computer: 15-bit addresses. → 2^{15} memory locations.

Each location stores 1 word = 16 bits.

→ $2^{15} \cdot 2^4 = 2^{19}$ bits.

1 byte = 8 bits. → 2^{19} bits = 2^{16} bytes.

1 KB (technically, "kibibyte" (KiB)) = 1024 = 2^{10} bytes.

So 2^{16} bytes = 2^6 KB = 64 KB. — $\frac{1}{2}$ for screen, $\frac{1}{2}$ for memory.

32-bit addresses = _____ memory?


$$2^{32} \text{ bytes} = 2^{22} \text{ KB} = 2^{12} \text{ MB} = 2^2 = 4 \text{ GB.}$$

64-bit addresses ?


$$2^{64} \text{ bytes} = 2^{54} \text{ KB} = 2^{44} \text{ MB} = 2^{34} \text{ GB} = 2^{24} \text{ TB} = 2^{14} \text{ PB} \\ = 2^4 \text{ EB}$$

Project 3

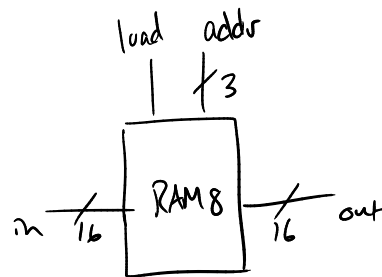- Bit = DFF
- Register = 16 bits.
- RAM - build by stages.
 - RAM8 - 8 registers.



- RAM64 - 8 RAM8.

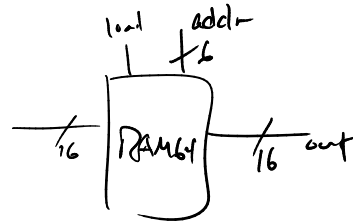

etc.

- PC (program counter).

